



**Figure 1** The autozeroed instrumentation amp, digitally programmable for voltage gains of three and 10, can help you to overcome the current inavailability of monolithic ICs for this task.

