



Figure 1 A buffer-amplifier circuit with a capacitive load can be marginally stable (a) or very stable (b). Keep the rate of closure between the open-loop-gain, A_{OL} , and the closed-loop-gain, A_{CL} , slope at 20 dB/decade.