



Figure 1 With Chipplexing, you need to add only N cheap, bipolar transistors to simultaneously drive two LEDs.