



Figure 1 This instrumentation amplifier serves two purposes: It forms a current-to-voltage converter having a transresistance of  $-5R$ , and it exerts a voltage drop of opposite polarity at point B, resulting in a zero potential at Input A, regardless of input-current  $I/O$ .