



Figure 2 This circuit converts the pulses from the Hall-effect IC into a dc voltage that the most basic voltmeter can read.