



Figure 4 To gauge the current matching from string to string in a 4×4 series-parallel array, this test circuit uses 16 LEDs from the same forward-voltage bin, which a 4A benchtop power supply drives. Experimenters repeated the test with randomly selected LEDs from four forward-voltage bins.