



Figure 2 This maximum-power-point-tracking controller relies on the well-known logarithmic behavior of transistor junctions.