



Figure 1 By placing a 10-k Ω resistor between a buffer op amp and a SAR-ADC input, you can see the ADC charge-injection action.