



Figure 1 A charge-pump circuit creates the boosted voltage to light LEDs for a flashlight.