



**Figure 2** During the on time, current flows through the inductor and then charges the capacitor.