



Figure 5 The pulse amplifier includes a paralleled, Darlington-driven RF-transistor-output stage. Collector-voltage adjustment, or rise-time trim, peaks Q_4 to Q_6 F_T , and the input-RC network optimizes output-pulse purity. A low-inductance layout is mandatory.