



Figure 7 A complete diode-forward-turn-on-time-measurement arrangement includes a subnanosecond rise-time pulse generator, pulse amplifier,  $Z_0$  probe, and 1-GHz oscilloscope.