



Figure B The pulse generator's waveforms include the clock (Trace A),  $Q_2$ 's collector ramp (Trace B), the trigger output (Trace C), and the pulse output (Trace D). The delay sets the output pulse approximately 170 nsec after the trigger output.

---