



Figure 1 The behavior of the RC topology is still simple when you replace R with an active circuit that synthesizes a negative resistance.