



Figure 1 Connecting optical feedback by opto-MOSFET IC₂ in the power-MOSFET-driver IC₁ stabilizes the high-side output voltage to 13.5V at values of loading current down to 3.7 mA. The power efficiency of the circuit increases for a loading current of less than 7 mA.