



Figure 2 To continue using switches with the same voltage range as that of Figure 1, you must add two switches and two independent control-logic blocks.