



**Figure 2** Adding a few components turns the current-limiting circuit into a pulser that reduces heat in the pass transistor,  $Q_2$  (a). The circuit's waveforms show the relationship between the input voltage and the load voltage (b).