



**Figure 1** The RC filter along with  $I/O_2$ 's interrupt-on-change feature provides a simple and cost-effective approach for a variety of time-scale measurements from microseconds to minutes.