



Figure 1 You can use a small-signal MOSFET to provide overvoltage-signal conditioning.