



Figure 1 This circuit for an SOC-differential-clock source drives two DDR chips.