



Figure 1 This simple circuit displays four states on four LEDs.