



Figure 1 A buck converter provides current sufficient to drive a high-brightness LED.