



Figure 1 A basic buck converter uses a PWM controller and a MOSFET.