



Figure 1 Transistors boost the output voltage and current of optoisolators, making an isolated amplifier output.