



Figure 2 Positive feedback from amplifier  $A_1$  causes  $C_1$  to increase in voltage, which exponentially amplifies the input voltage.