



Figure 1 You can build an instrumentation amp operating from a single supply that permits you to reset the system offset by applying a positive-correction voltage to the V_{REF} input.