



**Figure 1** For a hysteretic buck-LED driver driving three LEDs in series, you must measure the anode and cathode voltages of the string when the Dim pin is high.