



Figure 1 This circuit controls a device through a relay and an intermittent buzzer with only one digital-I/O pin.