



Figure 2 A Spice simulation of the buzzer circuit replaces the buzzer with 50Ω resistance and plots the current through the buzzer and the status of the I/O line.