



FIGURE 1 This buck-boost circuit regulates a constant LED current with a negative output voltage.