



**FIGURE 2** Shorting the soft-start capacitor to ground allows the PWM drive (top) to dim the LED by decreasing its current (bottom). For applications that don't require high-speed response or 100% PWM dimming, this method may suffice.