



FIGURE 1 Power Integrations based this tapped-buck power supply on the LNK605DG switching IC, which uses just 16 components. This circuit operates over an input-voltage range of 85 to 265V ac, enabling the use of one lamp worldwide.