



FIGURE 2 This 9W LED driver uses a valley-fill circuit for an improved power factor, which a draft version of the Energy Star requirements for solid-state lighting requires.