



Figure 13 Ensuring that no bad-cell reading is misinterpreted as a good cell requires some type of open-wire detection, such as temporarily turning on the passive-balancing circuit. If the cell connection is open, the measured voltage will be zero.