



**Figure 1** In the complementary-differential-input-stage topology, when the amplifier's inputs are near the negative rail, the PMOS transistors are on, and the NMOS transistors are off.