



Figure 1 To calculate Thevenin-equivalent circuits, you first choose a load resistance— $2\text{ k}\Omega$ in this circuit.