



Figure 1 After you press and release S₁ 23 times, the DAC produces a constant-4-mA-current output.