



Figure 1 A two-IC circuit converts a -5V input to a 3.3V output.