



Figure 1 A dc/dc regulator is a linear system with feedback. You model it as a classical feedback system with a transfer function relating the output voltage to the reference voltage.

---