



Figure 2 You make a conventional Sallen-Key filter using an op amp and two RC networks.

---