



Figure 5 Adding a voltage-follower amplifier to the feedback loop does not affect the transfer function but does remove the interaction of the input with the amplifier's output impedance. This approach drastically reduces the stopband peaking.