



Figure 6 Lowpass filtering within the loop attenuates secondary stopband leakage at higher frequencies. Set R_3 , R_4 , C_3 , and C_4 to cut off about 100 times the filter-design frequency but less than the 3-dB bandwidth of A_2 .