



Figure 8 In the bench results for the circuit of Figure 7, the addition of A_2 improves the stopband performance by more than 40 dB at three decades past the 10-kHz break-point frequency.
