



Figure 1 A sump-pump controller uses a quad-NAND gate to drive a solid-state relay.