



Figure 2 Connecting the potentiometer to NAND Gate B creates a water-level controller.