



Figure 1 This simple MAX IIZ circuit uses an LED as an emitter and a sensor.