



Figure 3 The circuit in Figure 2 provides a wide output range, output current that is directly proportional to the input voltage, and high linearity and precision.