



Figure 1 Passing current through a MOSFET and regulating it with a current-sense monitor bypasses the BCD switches, letting you increase load current.