



Figure 1 An oscilloscope snapshot shows the base voltages of Q_1 and Q_2 in figures 2 and 3.