



Figure 2 This circuit drives low-power, unipolar stepper motors using only shift-register IC<sub>1</sub> and a few resistors and transistors.